CONTADOR DE DÉCADA PRÁCTICA #5

• MOD 10 (0-9)

#	ESTADO ANTERIOR	ESTADO SIGUIENTE	EC. DE ENTRADA A LOS	SALIDAS
	(Y)		F-F´S D D D D	ABCDEFG
0	0 A	А		0000001
1	0 B	В		1001111
2	0 C	С		0010010
3	0 D	D		0000110
4	0 E	E		1001100
5	0 F	F		0 1 0 0 1 0 0
6	0 G	G		0100000
7	0 H	Н		0001111
8	0 1	I		0000000
9	0 J	J		0001100
1	1 A	В		1001111
2	1 B	С		0010010
3	1 C	D		0000110
4	1 D	Е		1001100
5	1 E	F		0100100
6	1 F	G		0 1 0 0 0 0 0
7	1 G	Н		0 0 0 1 1 1 1
8	1 H	I		000000
9	1 I	J		0001100
0	1 J	Α		0000001

TABLA DE EXITACIÓN

Qt	Qt+1	D
0	0	0
0	1	1
1	0	0
1	1	1

								Qt	+1					
#	,	Y Q	t3 (Qt2	Qt1	Qt0	 Q3	Q2	Q1	Q0	D3	D2	D1	D0
0		0	0	0	0	0	0	0	0	0	0	0	0	0
1		0	0	0	0	1	0	0	0	1	0	0	0	1
2		0	0	0	1	0	0	0	1	0	0	0	1	0
3		0	0	0	1	1	0	0	1	1	0	0	1	1
4		0	0	1	0	0	0	1	0	0	0	1	0	0
5		0	0	1	0	1	0	1	0	1	0	1	0	1
6		0	0	1	1	0	0	1	1	0	0	1	1	0
7		0	0	1	1	1	0	1	1	1	0	1	1	1
8		0	1	0	0	0	1	0	0	0	1	0	0	0
9		0	1	0	0	1	1	0	0	1	1	0	0	1
10		0	1	0	1	0	X	X	X	X	Х	X	X	X
11		0	1	0	1	1	Х	X	X	Χ	Х	Χ	X	X
12		0	1	1	0	0	Х	X	X	Χ	Х	Χ	X	X
13		0	1	1	0	1	Χ	X	Χ	Χ	Х	Χ	X	X
14		0	1	1	1	0	Х	Х	Х	Х	Х	Χ	Х	X
15		0	1	1	1	1	Х	X	X	Χ	Х	Χ	X	X
16		1	0	0	0	0	0	0	0	1	0	0	0	1
17		1	0	0	0	1	0	0	1	0	0	0	1	0
18		1	0	0	1	0	0	0	1	1	0	0	1	1
19		1	0	0	1	1	0	1	0	0	0	1	0	0
20		1	0	1	0	0	0	1	0	1	0	1	0	1
21		1	0	1	0	1	0	1	1	0	0	1	1	0
22		1	0	1	1	0	0	1	1	1	0	1	1	1
23		1	0	1	1	1	1	0	0	0	1	0	0	0
24		1	1	0	0	0	1	0	0	1	1	0	0	1
25		1	1	0	0	1	0	0	0	0	0	0	0	0
26		1	1	0	1	0	Х	Х	X	Х	Х	Χ	X	Х
27		1	1	0	1	1	Х	Χ	X	Х	Х	Χ	X	X
28		1	1	1	0	0	Х	Х	X	Х	Х	Χ	Х	X
29		1	1	1	0	1	Х	Х	X	Х	Х	Χ	X	Х
30		1	1	1	1	0	Х	Χ	X	Х	Х	Χ	X	X
31		1	1	1	1	1	Х	Х	X	Х	Х	Х	X	Х

MAPAS DE KARNAUGH

• **D3=** Em(8,9,23,24) + D.C (10,11,,12,13,14,15,26,27,28,29,30,31)

Q1 Q0 Q3 Q2	00	01	11	10		
00						
01						
11	X	X	X	X		
10	1	1	X	X		
Y′						

Q1 Q0 Q3 Q2	00	01	11	10
00				
01			1	
11	Х	Х	Х	X
10	1		X	Х

D3= y' Q3 + y Q2 Q1 Q0 + Q3Q0

• **D2=** Em(4, 5, 6, 7, 19, 20, 21, 22) + D.C (10,11,,12,13,14,15,26,27,28,29,30,31)

Q1 Q0 Q3 Q2	00	01	11	10
00				
01	1	1	1	1
11	Х	X	X	X
10			X	Х

Q1 Q0 Q3 Q2	00	01	11	10
00				
01	1	1		1
11	X	Х	Х	Х
10			Х	X

D2= y'Q2 + y Q1 Q2 + y Q0 Q2

• **D1=** Em(2, 3, 6, 7, 17, 18, 21, 22) + D.C (10,11,12,13,14,15,26,27,28,29,30,31)


Q1 Q0 Q3 Q2	00	01	11	10			
00			1	1			
01			1	1			
11	X	X	Х	Х			
10			Х	Х			
Υ΄							

Q1 Q0 Q3 Q2	00	01	11	10
00		1		1
01		1		1
11	X	Х	Х	X
10			X	Х
		Υ		

D1= y'Q1 + y Q1 Q0 + y Q1 Q0 Q3

• **D0=** Em(1, 3, 5, 7,9,16,18,20,22,24) + D.C (10,11,12,13,14,15,26,2,28,29,30,31)

Q1 Q0 Q3 Q2	00	01	11	10		
00		1	1			
01		1	1			
11	X	Х	Х	X		
10		1	Х	X		
v ′						

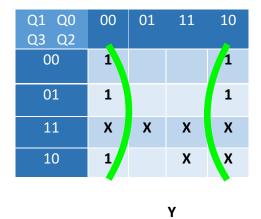

D0= y'Q0 + y Q0 Q3